 



Time and Storage

Time




- Synchronization:
 - Wait for the output of all adders to be valid before propagating result
 - Estimate computation time to find appropriate delay
 - Insert « barriers » to synchronize outputs
- Control of « barriers »: **clock**, periodic signal

Why do you need Time ?

 


- Synchronization:
 - Wait for the output of all adders to be valid before propagating result
 - Estimate computation time to find appropriate delay
 - Insert « barriers » to synchronize outputs
- Control of « barriers »: **clock**, periodic signal

Why do you need Memory ?

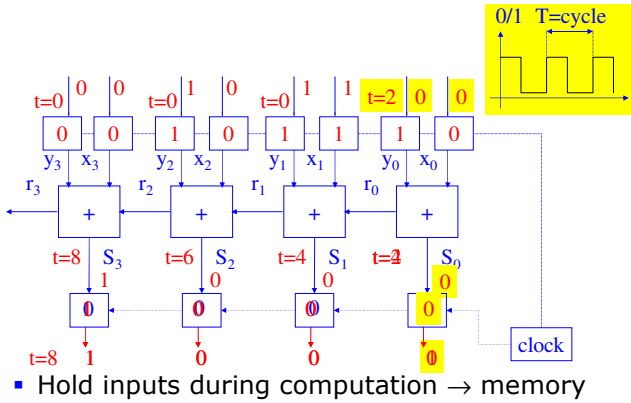


How To Implement A Memory Circuit ?

C	X	Z(t)	Z(t+Δt)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 


$$Z(t + \Delta t) = C \cdot Z(t) + X \cdot Z(t) + C \cdot X$$

 - Barrier: input X, output Z, control using clock C:
 - C=0: memory → Z(t+Δt) = Z(t)
 - C=1: propagate information → Z(t+Δt) = X
- Loop: send output to input → **memory**



Latches

 


Latch SR

S	R	Q	Q+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	d
1	1	1	d


- Memorization circuits used as "building blocks"
- Different types of latches (number of control signals and behavior)
- SR= Set/Reset: memorize or set 1/0.

Latches

 

C	D	Q	Q'
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


 
- Latch D: *Delay*, memorization circuit only
- Adding clock:
 - C=0 → memorization
 - C=1 → open



Flips-Flops


- Operators/Computations usually in sequence
- A latch can store a result but not truly separate two operators

1-bit adder delay

  

Flips-Flops

Flip-Flop D

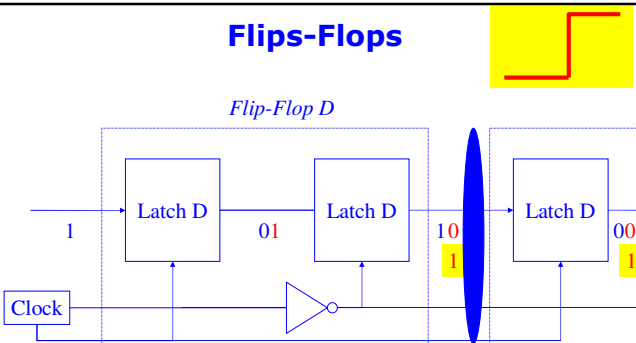

- Connect two latches, open on opposite clock phases:
 - ⇒ The signal can only go through one of the two latches (≈ air lock).

