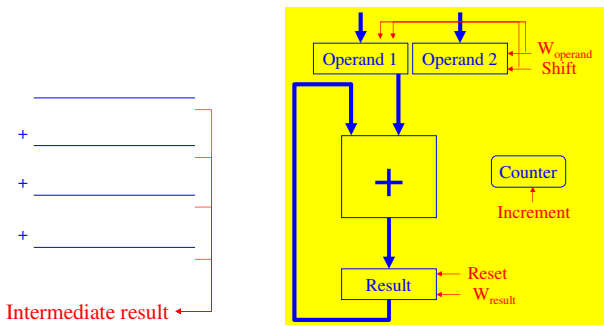



Control

Control




- Example with sequential multiplication


Multiplier Control

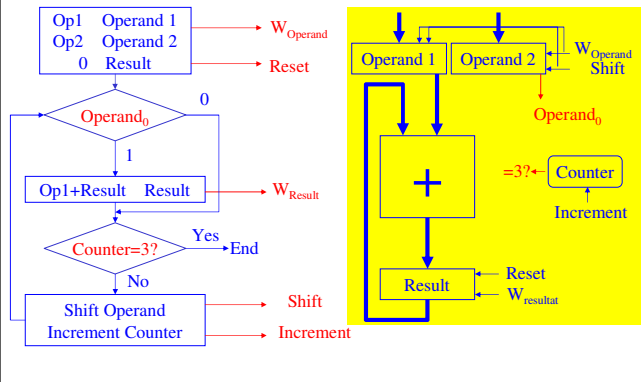

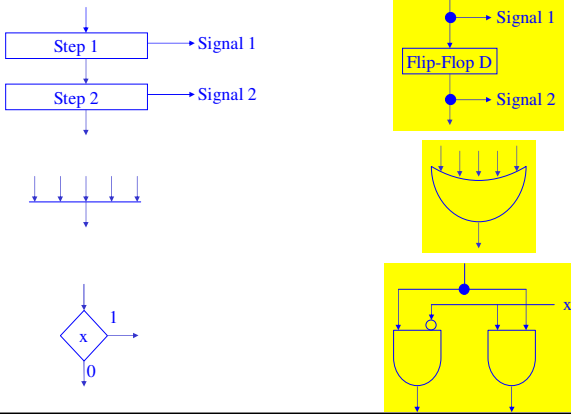
Converting a Flowchart into a Control Circuit




Multiplier Control Circuit

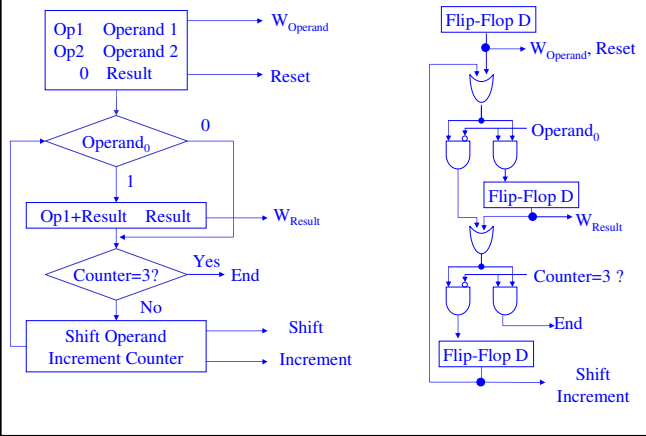

Multiplier Control Circuit

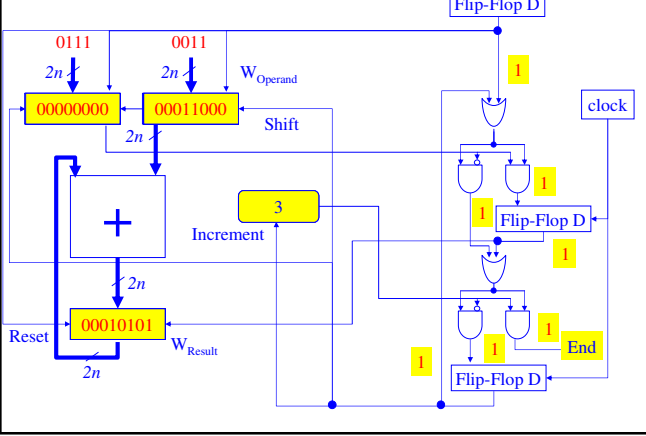

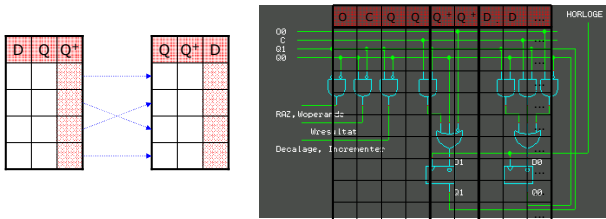Sequential Circuit Design – Final Circuit



- Using D flip-flops
- Set D_1, D_0 so as to impose desired transitions
- $Q^+ = D$ transition table = truth table of D_1, D_0 .
- Outputs correspond to current states

$$D_1 = Q_1 + Q_0 + C \cdot Q_1$$


$$D_0 = Q_1 \cdot Q_0 + Q_1 \cdot Q_1 + C \cdot Q_1$$

$$W_{operand} = \text{Reset} = Q_1 \cdot Q_0$$

$$W_{res} = Q_1 \cdot Q_0$$

$$\text{Shift} = \text{Increment} = Q_1 \cdot Q_0$$


Data Paths - Bus

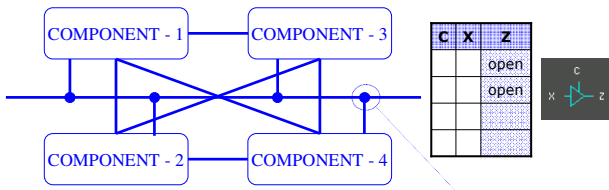

- Connecting a large number of components: **bus**.
- Bus = a set of n -bit wires
- Very cheap, but not efficient with large number of components



Bus

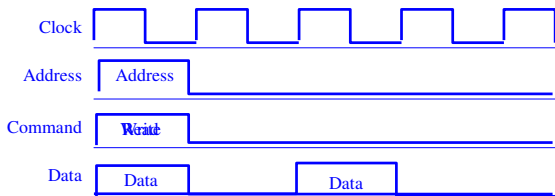

- Synchronous buses:
 - All components timed with same clock
 - Links indicate **address, data, command**
 - Internal buses or connection to memory
- Access protocol (priorities,...) implemented in control circuit
